

**CSE 4207 CT 4 Assignment**  
**Roll No: 1903077**

**Assignment Problem:**

**Category: C**

**Word Size = 7**

**ALU Operations = AND, ADD**

**Solution:**

**Video:**

<b>Have you uploaded the video?</b>	YES
<b>Check List 1:</b> Have you explained the design using testbenches to prove that your circuit is working correctly and giving correct results?	YES
<b>Check List 2:</b> Have you shown full synthesis results showing all the required info including RTL Synthesis, RTL Floorplan, RTL Power Analysis, GDS and Heatmap (for details, see assignment template doc)?	YES
<b>NB: Failing to upload video will cause heavy point penalty (5-6 Marks)</b>	
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

**HDL Code:**

<b>Check List:</b> Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, CONTROLLER, TOP, TOP_TESTBENCH, ALU_TESTBENCH, CONTROLLER_TESTBENCH?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

**top.v**

```
`include "controller.v"

module Top (
    input wire clk,
    input wire rst,
    output wire [6:0] res,
    output wire CF,
    output wire GZ // Greater than zero flag
);

Controller uut0(
    .clk(clk),
```

```

        .rst(rst),
        .res(res),
        .CF(CF),
        .GZ(GZ)
    );

endmodule

```

## controller.v

```

`include "alu_7_bit.v"

module Controller (
    input clk, rst,
    output reg [6:0] a,
    output reg [6:0] b,
    output reg op,

    output wire [6:0] res,
    output wire GZ, //grater than zero flag
    output wire CF
);

    ALU uut0(

        .a(a),
        .b(b),
        .op(op),
        .res(res),
        .GZ(GZ),
        .CF(CF)
    );

    localparam start =3'b000,
               one=3'b001,
               two=3'b010,
               three=3'b011,
               finish=3'b100;

    reg [2:0] current_state, next_state;

    always @(posedge clk)
    begin

```

```

    if(rst)
    begin
        current_state<=start;
    end
    else
    begin
        current_state<=next_state;
    end
end

always @(*)
begin
    case (current_state)
        start:
        begin
            a=7'b0000000;
            b=7'b0000000;
            op=0;
            next_state=one;
        end
        one:
        begin
            a=7'b0000000;
            b=7'b1111111;
            op=0;
            next_state=two;
        end
        two:
        begin
            a=7'b1101101;
            b=7'b1111111;
            op=1;
            next_state=three;
        end

        three:
        begin
            a=7'b1101101;
            b=7'b0100110;
            op=0;
            next_state=finish;
        end

        finish:
        begin
            a=7'b0000000;
            b=7'b0000000;
            op=0;

```

```

        next_state=finish;
    end
    default:
    begin
        a=7'b0000000;
        b=7'b0000000;
        op=0;
        next_state=start;
    end
endcase

end
endmodule

```


### RTL Timing Diagram:

**Check List:** Have you added all the timing diagrams of ALU\_TESTBENCH, CONTROLLER\_TESTBENCH, TOP\_TESTBENCH?


YES/NO

**NB:** Failing to add any required info will cause point penalty (1-2 Marks)

top\_tb.v

 

alu\_tb.v

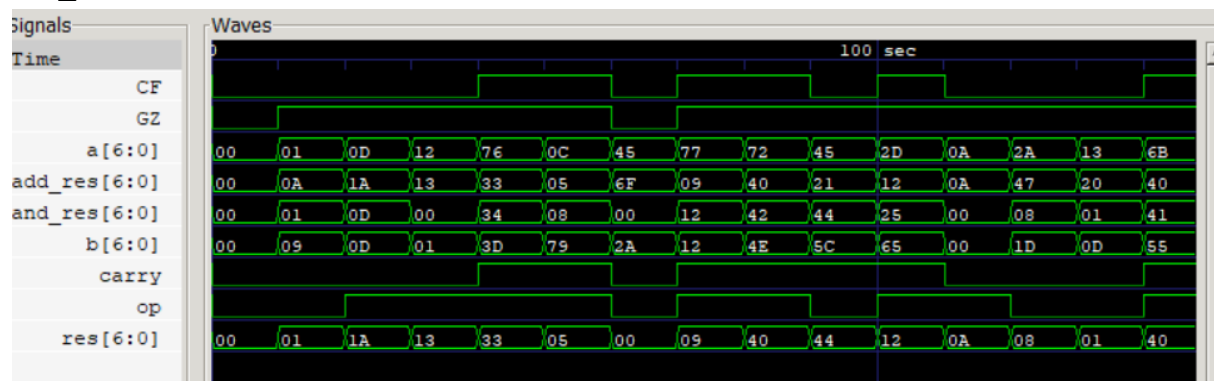

### RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

<b>Check List:</b> Have you added <i>RTL synthesis summary</i> , <i>RTL synthesized design figure</i> and <i>Standard cell usage in synthesized design</i> ?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	



RTL synthesis summary

```
120. Printing statistics.

=== Top ===

Number of wires:           53
Number of wire bits:       135
Number of public wires:    26
Number of public wire bits: 108
Number of ports:           5
Number of port bits:       11
Number of memories:        0
Number of memory bits:     0
Number of processes:       0
Number of cells:           42
$_ANDNOT_                  14
$_DFF_P_                   4
$_MUX_                     4
$_NOR_                     3
$_NOT_                     3
$_ORNOT_                   2
$_OR_                      5
$_XOR_                     3
$scopeinfo                 4
```

RTL synthesized design figure :

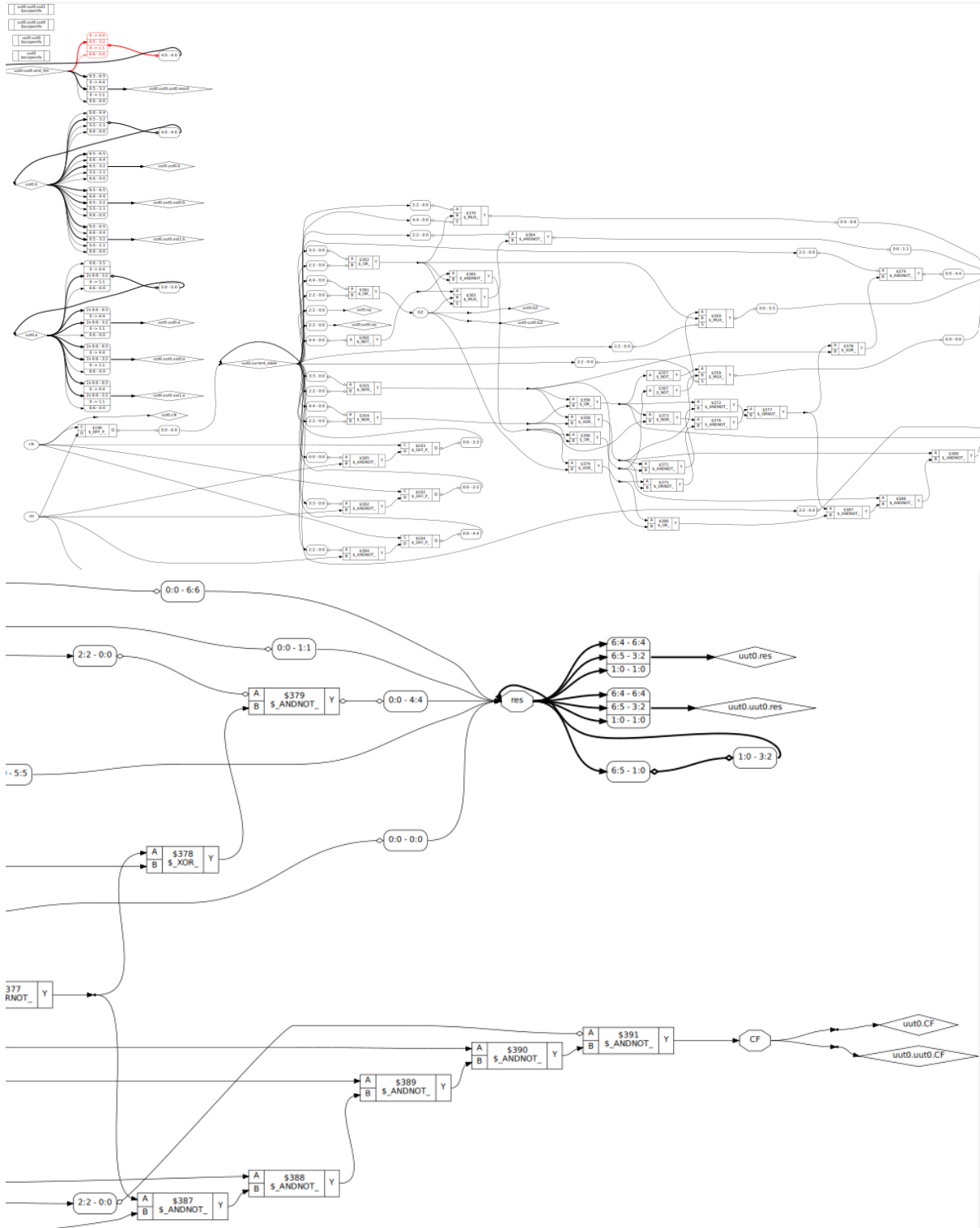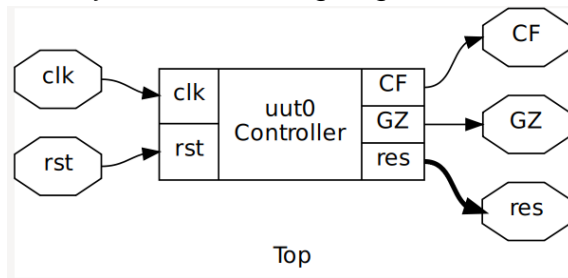

Standard cell usage in synthesized design

cells by Master

Cell	Count
sky130_ef_sc_hd_decap_12	33
sky130_fd_sc_hd_a2lo_1	1
sky130_fd_sc_hd_and2b_1	3
sky130_fd_sc_hd_and3b_1	1
sky130_fd_sc_hd_buf_1	1
sky130_fd_sc_hd_buf_2	7
sky130_fd_sc_hd_clkbuf_1	3
sky130_fd_sc_hd_clkbuf_16	3
sky130_fd_sc_hd_conb_1	2
sky130_fd_sc_hd_decap_3	28
sky130_fd_sc_hd_decap_4	5
sky130_fd_sc_hd_decap_6	5
sky130_fd_sc_hd_decap_8	5
sky130_fd_sc_hd_dfxtp_1	4
sky130_fd_sc_hd_dlygate4sd3_1	3
sky130_fd_sc_hd_fill_1	15
sky130_fd_sc_hd_fill_2	4
sky130_fd_sc_hd_or2_1	2
sky130_fd_sc_hd_tapvpwrvgnd_1	12

Cells by SCL

SCL	Count
sky130_ef_sc_hd	33
sky130_fd_sc_hd	104

Buffers by Cell Master

Buffer	Count
sky130_fd_sc_hd_buf_1	1
sky130_fd_sc_hd_buf_2	7
sky130_fd_sc_hd_clkbuf_1	3
sky130_fd_sc_hd_clkbuf_16	3
sky130_fd_sc_hd_dlygate4sd3_1	3

### RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)

<b>Check List:</b> Have you added RTL Floorplan info?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

```
[INFO] Extracting DIE_AREA and CORE_AREA from the floorplan
[INFO] Floorplanned on a die area of 0.0 0.0 50.0 50.0 (µm).
[INFO] Floorplanned on a core area of 5.52 10.88 44.16 38.08 (µm).
Writing metric design__die__bbox: 0.0 0.0 50.0 50.0
Writing metric design__core__bbox: 5.52 10.88 44.16 38.08
Setting global connections for newly added cells...
[INFO] Setting global connections...
Updating metrics...
Cell type report:
          Count      Area
Buffer           3      13.76
Sequential cell   4      85.08
Multi-Input combinational cell  9      65.06
Total           16     163.91
```

### RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)

<b>Check List:</b> Have you added RTL Power Analysis info?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

```
6-01_11-58-51/54-openroad-stapostpnr/nom_tt_025C_1v80/power.rpt


=====
report_power
=====
===== nom_tt_025C_1v80 Corner =====

Group              Internal Power    Switching Power    Leakage Power    Total Power (Watts)
-----
Sequential          6.717540e-06  1.757943e-07  3.312726e-11  6.893367e-06  20.5%
Combinational       1.026952e-06  1.635777e-06  1.062416e-10  2.662835e-06  7.9%
Clock               2.030187e-05  3.843450e-06  1.762912e-10  2.414550e-05  71.6%
Macro               0.000000e+00  0.000000e+00  0.000000e+00  0.000000e+00  0.0%
Pad                 0.000000e+00  0.000000e+00  0.000000e+00  0.000000e+00  0.0%
-----
Total               2.804637e-05  5.655021e-06  3.156601e-10  3.370170e-05  100.0%
                   83.2%      16.8%      0.0%
```

### GDS Layout (130nm Skywater PDK with OpenLane toolchain)



<b>Check List:</b> Have you added the GDS Layout figure?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

 

### Heatmap (130nm Skywater PDK with OpenLane toolchain)

<b>Check List:</b> Have you added the heatmap?	YES
<b>NB: Failing to add any required info will cause point penalty (1-2 Marks)</b>	

